

<b>Disciplina:</b> ELE1717 - Sistemas Digitais <b>Curso:</b> Engenharia Mecatrônica
--

## Material de suporte - Divisor de Clock

```
library ieee;
use ieee.std_logic_1164.all;

entity CLK_Div is
    port (clk_in : in  std_logic;
          clk_out: out std_logic);
end CLK_Div;

architecture ckt of CLK_Div is
    signal ax : std_logic;

begin
    process(clk_in)
        variable cnt: integer range 0 to 13500000 := 0;
    begin
        if (rising_edge(clk_in)) then
            if (cnt=13500000) then
                cnt:=0;
                ax <= not ax;
            else
                cnt:=cnt+1;
            end if;
        end if;
    end process;
    clk_out <= ax;
end ckt;
```

<b>Disciplina:</b> ELE1717 - Sistemas Digitais <b>Curso:</b> Engenharia Mecatrônica
--

## Material de suporte - Flip-Flop D


```
library ieee;
use ieee.std_logic_1164.all;

entity ffd is
    port (clk,d,p,c: in  std_logic;
          q          : out std_logic);
end ffd;

architecture ckt of ffd is
    signal qs: bit;
begin
    process(clk,p,c)
    begin
        if      p = '0' then qs <= '1';
        elsif  c = '0' then qs <= '0';
        elsif  clk='1' and clk'event then
            qs <= d;
        end if;
    end process;
    q <= qs;
end ckt;
```

**Disciplina:** ELE1717 - Sistemas Digitais  
**Curso:** Engenharia Mecatrônica
 
## Material de suporte - MDE do tipo Moore



```

library ieee;
use ieee.std_logic_1164.all;


entity mde_b is
    port (clk, r, w: in std_logic;
          z      : out std_logic);
end mde_b;

architecture ckt of mde_b is
    type state_type is (a, b, c);
    signal y_present, y_next : state_type;
begin
    process (w,y_present)
    begin
        case y_present is
            when a =>
                if w = '0' then y_next <= a;
                else y_next <= b; end if;
            when b =>
                if w = '0' then y_next <= a;
                else y_next <= c; end if;
            when c =>
                if w = '0' then y_next <= a;
                else y_next <= c; end if;
        end case;
    end process;

    process (clk,r)
    begin
        if r = '0' then
            y_present <= a;
        elsif (clk'event and clk = '1') then
            y_present <= y_next;
        end if;
    end process;
    z <= '1' when y_present = c else '0';
end ckt;
  
```

**Disciplina:** ELE1717 - Sistemas Digitais  
**Curso:** Engenharia Mecatrônica
 
## Material de suporte - MDE do tipo Mealy



```

library ieee;
use ieee.std_logic_1164.all;

entity mde_d is
    port (clk, r, w: in std_logic;
          z      : out std_logic);
end mde_d;

architecture ckt of mde_d is
    type state_type is (a, b);
    signal y : state_type;
begin
    process (r, clk)
    begin
        if r = '0' then
            y <= a;
        elsif (clk'event and clk = '1') then
            case y is
                when a =>
                    if w = '0' then y<=a;
                    else y<=b; end if;
                when b =>
                    if w = '0' then y<=a;
                    else y<=b; end if;
            end case;
        end if;
    end process;

    process ( y, w )
    begin
        case y is
            when a => z <= '0';
            when b => z <= w;
        end case;
    end process;
end ckt;
  
```