

CSE140: Components and Design Techniques for Digital Systems

Register Transfer Level (RTL) Design

Instructor: Mohsen Imani

Slides from Tajana Simunic Rosing



CAPE

CAPEs are out!!!

<https://cape.ucsd.edu/students/>

Please submit your evaluations !!!!

**Your feedback is very important, please take
the time to fill out the survey.**

3D Xpoint Memory



About the final



~150 minutes Final Exam

Bring one 8 ½ x 11" paper with handwritten notes, but nothing else


Problems including (but not limited to):

- ALU design
- ALU components (shifters, adders, etc.)
- FSM
 - Moore, Mealy, design of FSM using state table, excitation table
- Timing constraints
- RTL design and HLSM



ALU: Arithmetic Logic Unit



Designing an Arithmetic Logic Unit

 

• ALU Control Lines (ALUOp)	Function
– 000	And
– 001	Or
– 010	Add
– 110	Subtract
– 111	Set-on-less-than


A One Bit ALU

  - This 1-bit ALU performs AND, OR, and ADD




A 32-bit ALU

1-bit ALU

 


32-bit ALU

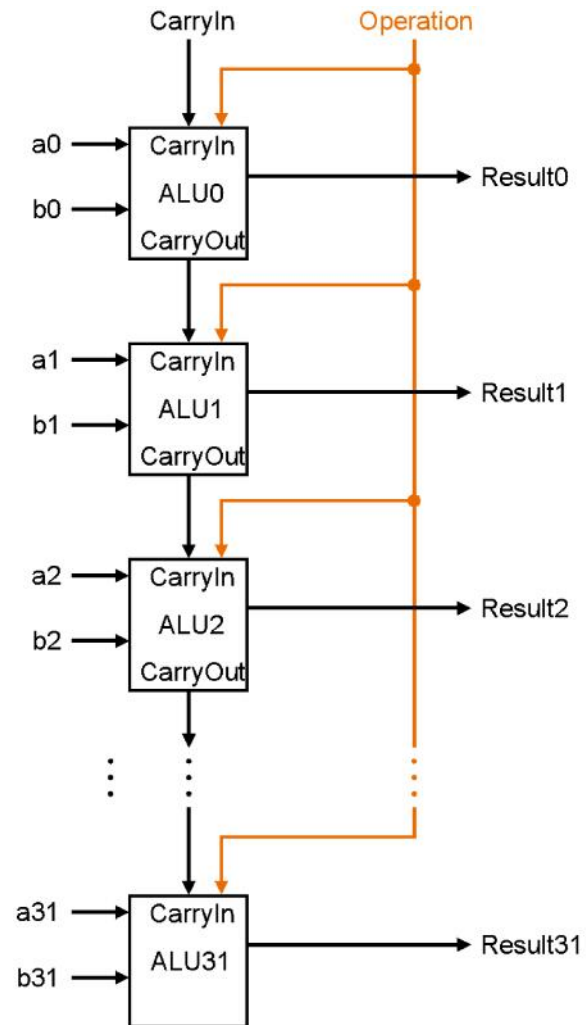



Subtract – We'd like to implement a means of doing A-B (subtract) but with only minor changes to our hardware. How?

1. Provide an option to use bitwise NOT A
2. Provide an option to use bitwise NOT B
3. Provide an option to use bitwise A XOR B
4. Provide an option to use 0 instead of the first CarryIn
5. Provide an option to use 1 instead of the first CarryIn

Selection	Choices
A	1 alone
B	Both 1 and 2
C	Both 3 and 4
D	Both 2 and 5
E	None of the above


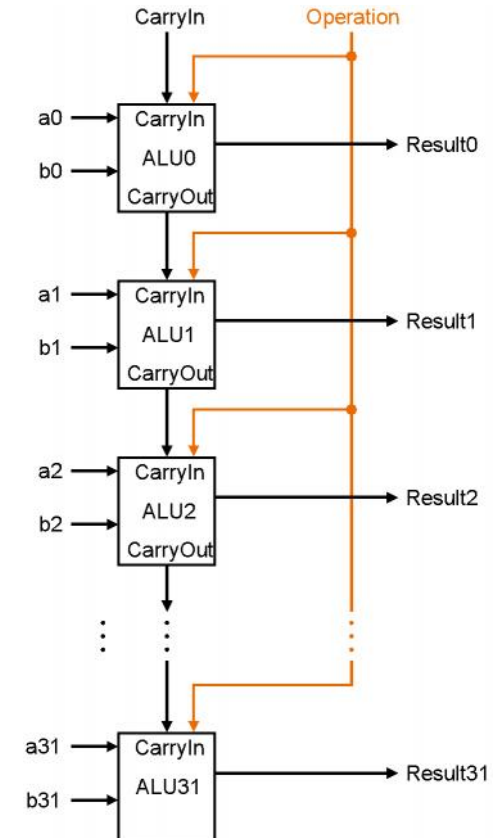


Full 32-bit ALU

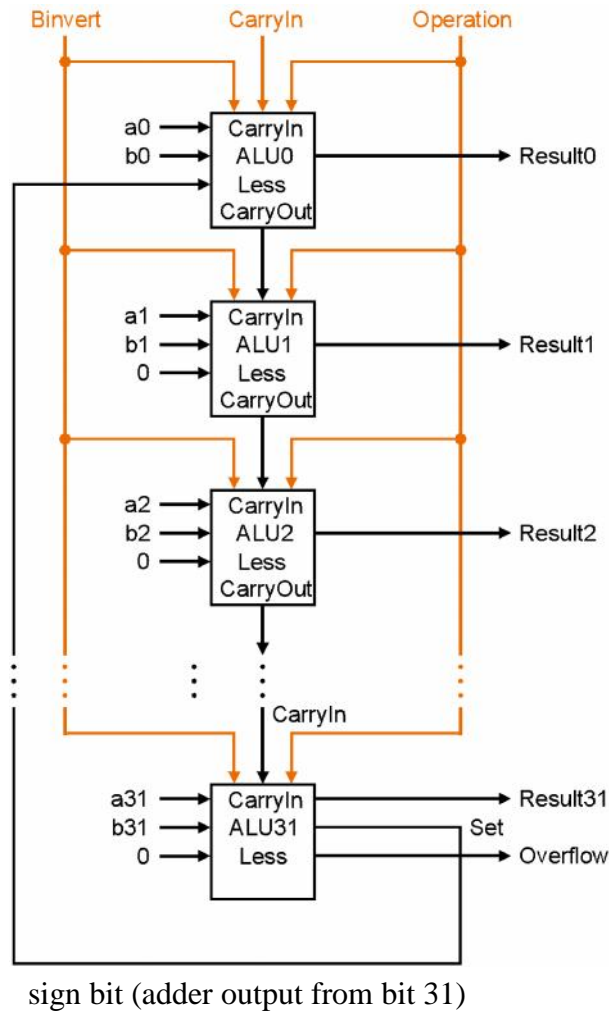 

what signals accomplish ADD?			
	Binvert	CIn	Oper
A	1	0	2
B	0	1	2
C	1	1	2
D	0	0	2
E	NONE OF THE ABOVE		

Full 32-bit ALU

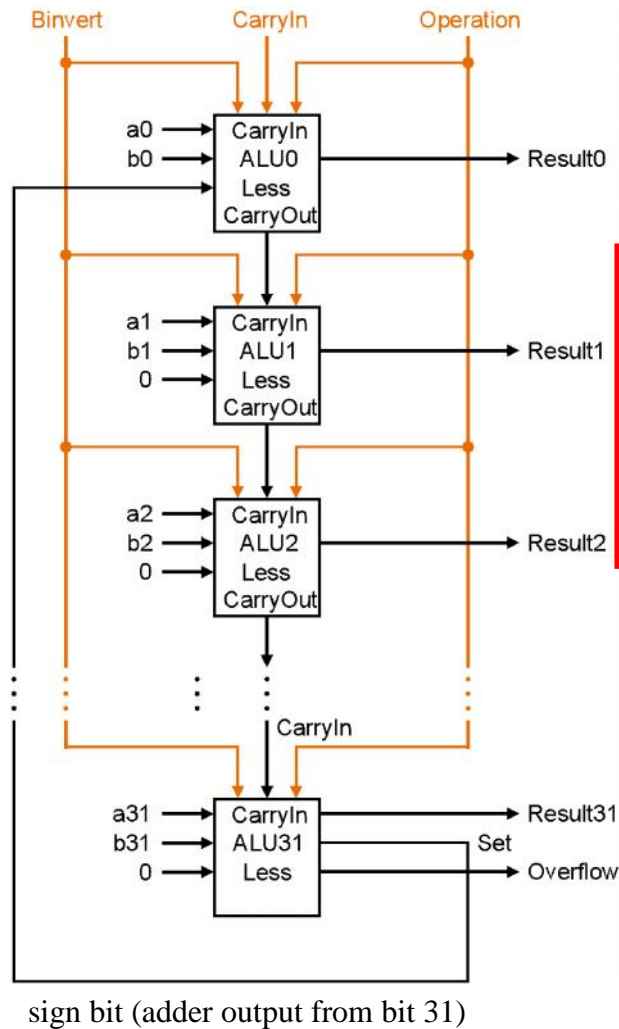
 


what signals accomplish OR?

	<u>Binvert</u>	<u>CIn</u>	<u>Oper</u>
A	1	0	0
B	0	1	1
C	1	1	0
D	1	0	1
E	NONE OF THE ABOVE		

Full 32-bit ALU

Little more intense –
can you get this?

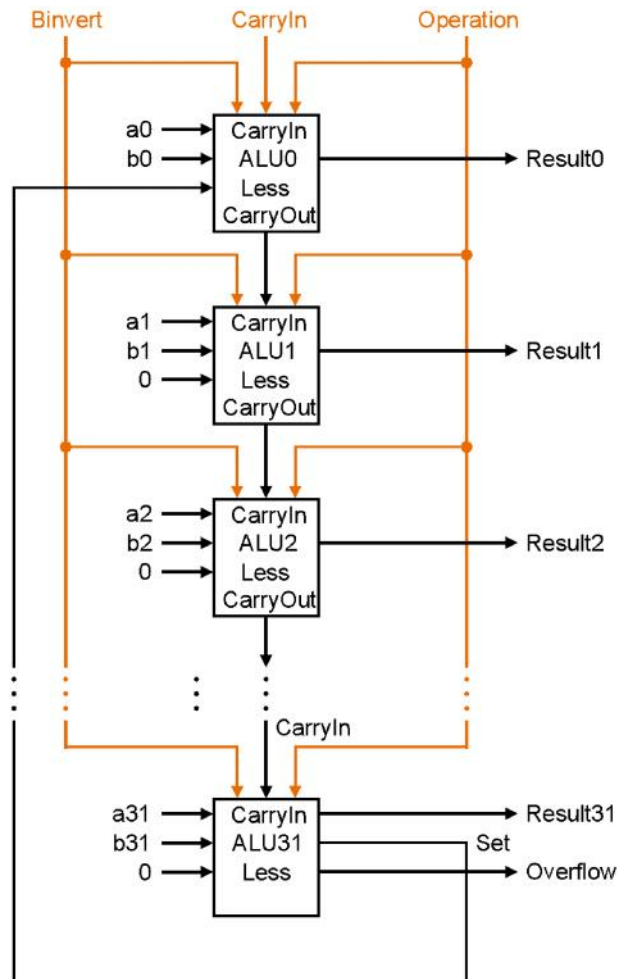
 


sign bit (adder output from bit 31)

what signals accomplish SUB?

	Binvert	CIn	Oper
A	1	0	2
B	0	1	2
C	1	1	2
D	0	0	2
E	NONE OF THE ABOVE		

Arithmetic Logic Unit – Example 2

  

F _{2:0}	Function
000	A & B
001	A B
010	A + B
011	Not used
100	A & ~B
101	A ~B
110	A - B
111	Not used


ALU Problem

x	y	z	OP
0	0	0	$A + B$
0	0	1	$A - B$
0	1	0	$A + A$
0	1	1	$A < B$
1	0	0	$A * 4$
1	0	1	$A / 4$
1	1	0	Reverse (A)
1	1	1	2-complement (B)

Design an ALU with two 8-bit inputs A and B that has three control bits xyz and implements the operations described in the table


ALU Problem

x	y	z	OP
0	0	0	A + B
0	0	1	A - B
0	1	0	A + A
0	1	1	A < B
1	0	0	A * 4
1	0	1	A / 4
1	1	0	Reverse (A)
1	1	1	2-complement (B)

 


ALU Problem

x	y	z	OP
0	0	0	A + B
0	0	1	A - B
0	1	0	A + A
0	1	1	A < B
1	0	0	A * 4
1	0	1	A / 4
1	1	0	Reverse (A)
1	1	1	2-complement (B)

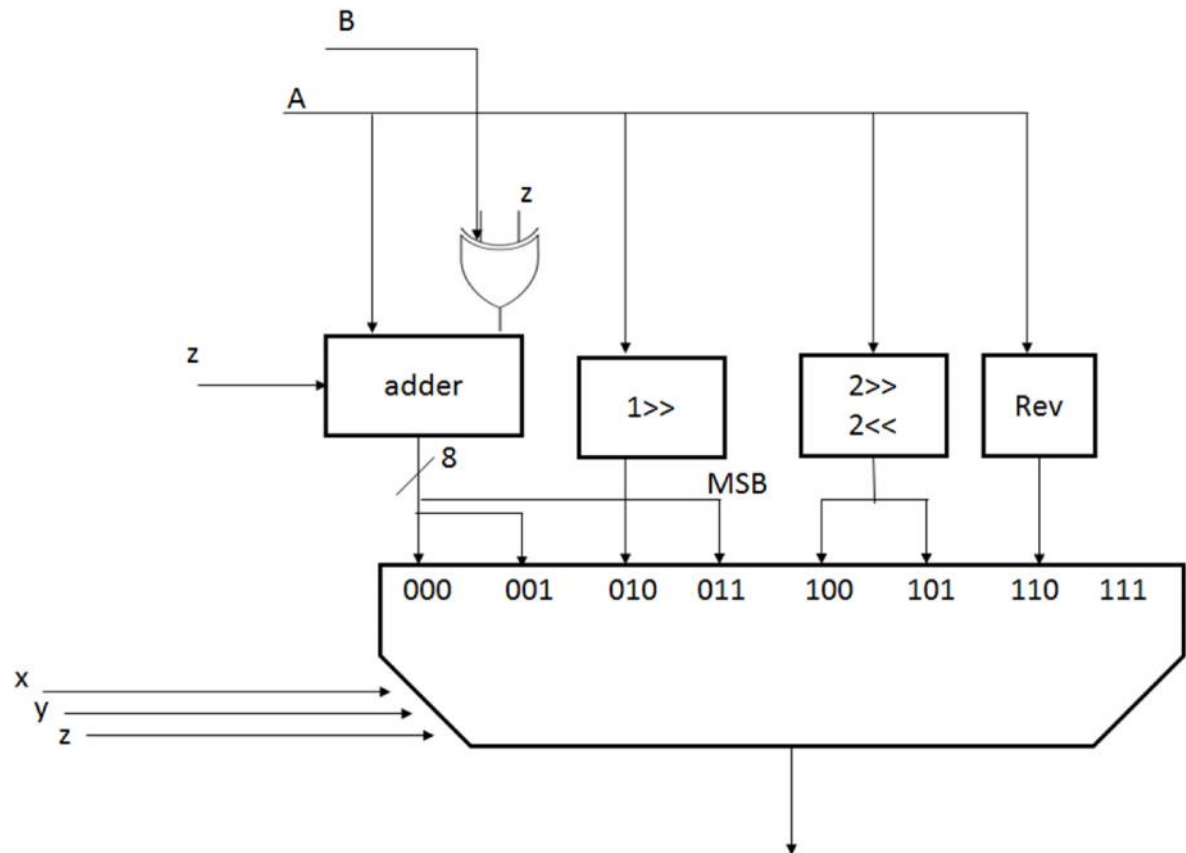


ALU Problem

x	y	z	OP
0	0	0	A + B
0	0	1	A - B
0	1	0	A + A
0	1	1	A < B
1	0	0	A * 4
1	0	1	A / 4
1	1	0	Reverse (A)
1	1	1	2-complement (B)

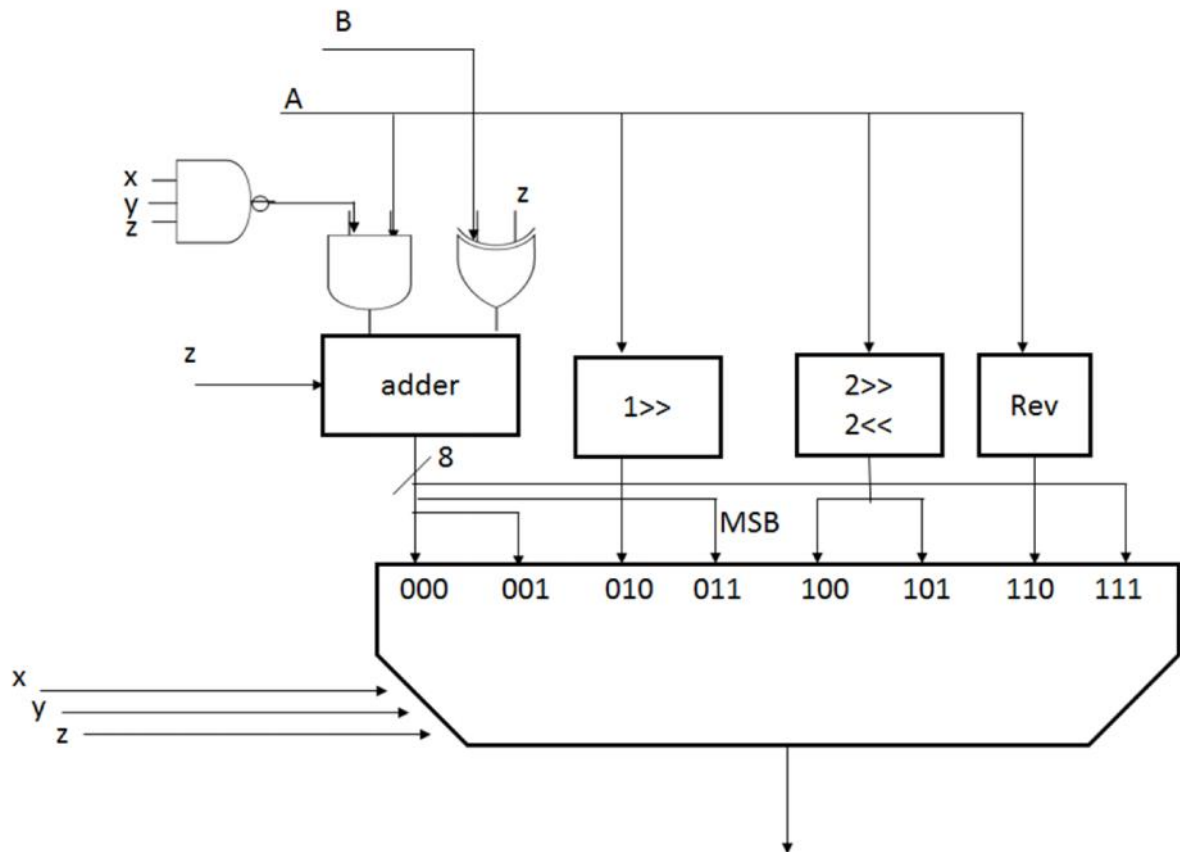

Design of a new FF (waveforms)

 


Q(t)	x	Q(t+1)
0	0	
0	1	
1	0	
1	1	


Design of a new FF

$$Q(t+1) = Q(t)'x' + Q(t)x$$


Q(t)	x	Q(t+1)
0	0	1
0	1	0
1	0	0
1	1	1

 

 Problem: FSM from circuit to state diagram



 Problem: FSM from circuit to state diagram



$D0 =$
 $y =$


Q0 a	D0	y
00		
01		
10		
11		

Qo \ a	0	1
0		
1		

Problem: FSM from circuit to state diagram


$$D0 = Q0' * a'$$

$$y = Q0 + a$$

 

Q0 a	D0	y
0 0	1	0
0 1	0	1
1 0	0	1
1 1	0	1

Qo \ a	0	1
0	1,0	0,1
1	0,1	0,1

 


Problem: FSM from word description to state diagram

A microwave oven has 3 modes of operation when it is on: High temperature (H), Low temperature (L) and Defrost (D). A 1-bit input signal X is controlled by a button. Whenever the button is pressed, X changes its value. When the oven is off, $X = 1$ will make it switch on to D mode. After that, every time X changes its value, the oven goes to L, then H the off again.


- Is it a Moore or a Mealy machine ?
- How many states does it have? How many bits are required to represent them?
- Draw the state diagram




Solution

 


Solution

 

Solution

 

 
Problem: FSM from state diagram to circuit



Q1Q0A	0	1
00	00, 1	10, 1
01	00, 0	00, 0
10	11, 0	11, 0
11	01, 1	11, 0

Q1Q0 A	D1	D0	Y
000	0	0	1
001	1	0	1
010	0	0	0
011	0	0	0
100	1	1	0
101	1	1	0
110	0	1	1
111	1	1	0

Solution

 

Q1Q0A	0	1
00	00, 1	10, 1
01	00, 0	00, 0
10	11, 0	11, 0
11	01, 1	11, 0

Q1Q0 A	D1	D0	Y
000	0	0	1
001	1	0	1
010	0	0	0
011	0	0	0
100	1	1	0
101	1	1	0
110	0	1	1
111	1	1	0

Solution

$$D0 = Q1$$

Q1 \ Q0A	00	01	11	10
0	0	0	0	0
1	1	1	1	1

$$D1 = Q1Q0' + Q1A + Q0'A$$


Q1 \ Q0A	00	01	11	10
0	0	1	0	0
1	1	1	1	0

$$Y = Q1'Q0' + Q1Q0A'$$

Q1 \ Q0A	00	01	11	10
0	1	1	0	0
1	0	0	0	1

Q1Q0 A	D1	D0	Y
000	0	0	1
001	1	0	1
010	0	0	0
011	0	0	0
100	1	1	0
101	1	1	0
110	0	1	1
111	1	1	0

Solution

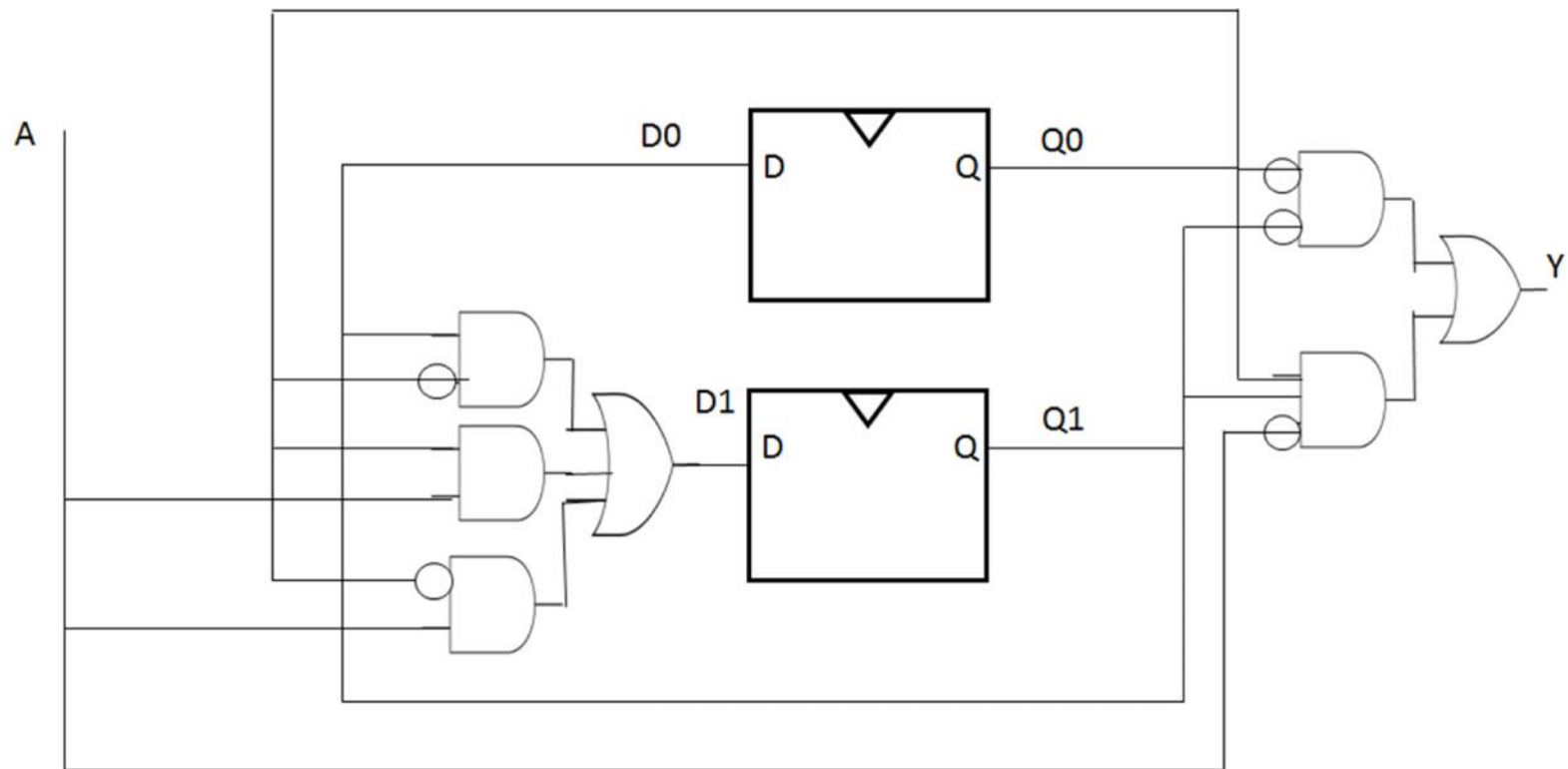

Circuit timing recap

Gate:

- minimum (contamination) delay : t_{cd}
- maximum (propagation) delay : t_{pd}

D-FF:

- Input:
 - Setup : t_{setup}
 - Hold : t_{hold}
- Output:
 - Minimum (contamination) delay : t_{ccq}
 - Maximum (propagation) delay : t_{pcq}



Time constraints

Setup time constraints:

$$T_c = t_{pcq} + t_{pd} + t_{setup}$$

Hold time constraints:

$$t_{hold} < t_{ccq} + t_{cd}$$

Time constraints with skew

Setup time constraints:

$$T_c \leq t_{pcq} + t_{pd} + t_{setup} + t_{skew}$$
$$t_{pd} \leq T_c - (t_{pcq} + t_{setup} + t_{skew})$$

Hold time constraints:

$$t_{ccq} + t_{cd} > t_{hold} + t_{skew}$$
$$t_{cd} > t_{hold} + t_{skew} - t_{ccq}$$

D-FF:

- t_ccq = 40
- t_pcq = 60
- t_setup = 70
- t_hold = 80

Gates:

AND:

- t_{pd} = 40
- t_{cd} = 30


OR:

- t_{pd} = 40
- t_{cd} = 30

NOT:

- t_pd = 30
- t_cd = 20

Timing constraints example

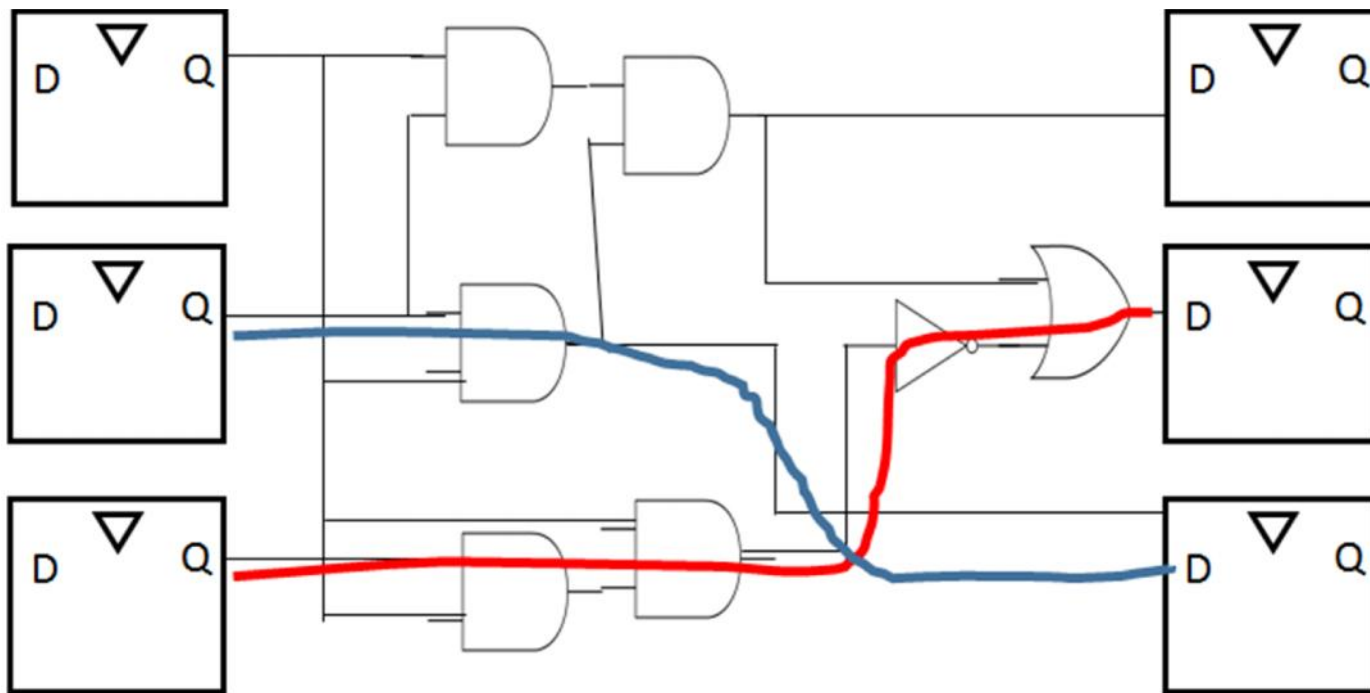

D-FF:

- $t_{ccq} = 40$
- $t_{pcq} = 60$
- $t_{setup} = 70$
- $t_{hold} = 80$

Gates:

AND:

- $t_{pd} = 40$
- $t_{cd} = 30$


OR:

- $t_{pd} = 40$
- $t_{cd} = 30$

NOT:

- $t_{pd} = 30$
- $t_{cd} = 20$

Timing constraints example

 

Setup time constraints:

$$T_c = t_{pcq} + t_{pd} + t_{setup}$$

$$T_c = (60) + (3 \cdot 40 + 30) + 70$$

$$T_c = 280\text{ps}$$


Hold time constraints:

$$t_{hold} < t_{ccq} + t_{cd}$$

$$80 < 40 + 30 \text{ ----> NO !!}$$

----> add buffer !

Timing constraints example

 

Setup time constraints with skew:

What is the maximum t_{skew} that can be tolerated before having a setup timing error with a frequency of 3 GHz?


$$T_c = 1 / f = 1 / 3\text{e}9 = 333\text{ps}$$


$$T_c = t_{\text{pcq}} + t_{\text{pd}} + t_{\text{setup}} + t_{\text{skew}}$$

$$333 - (60) - (3 \cdot 40 + 30) - 70 = t_{\text{skew}}$$

$$53\text{ps} = t_{\text{skew}}$$

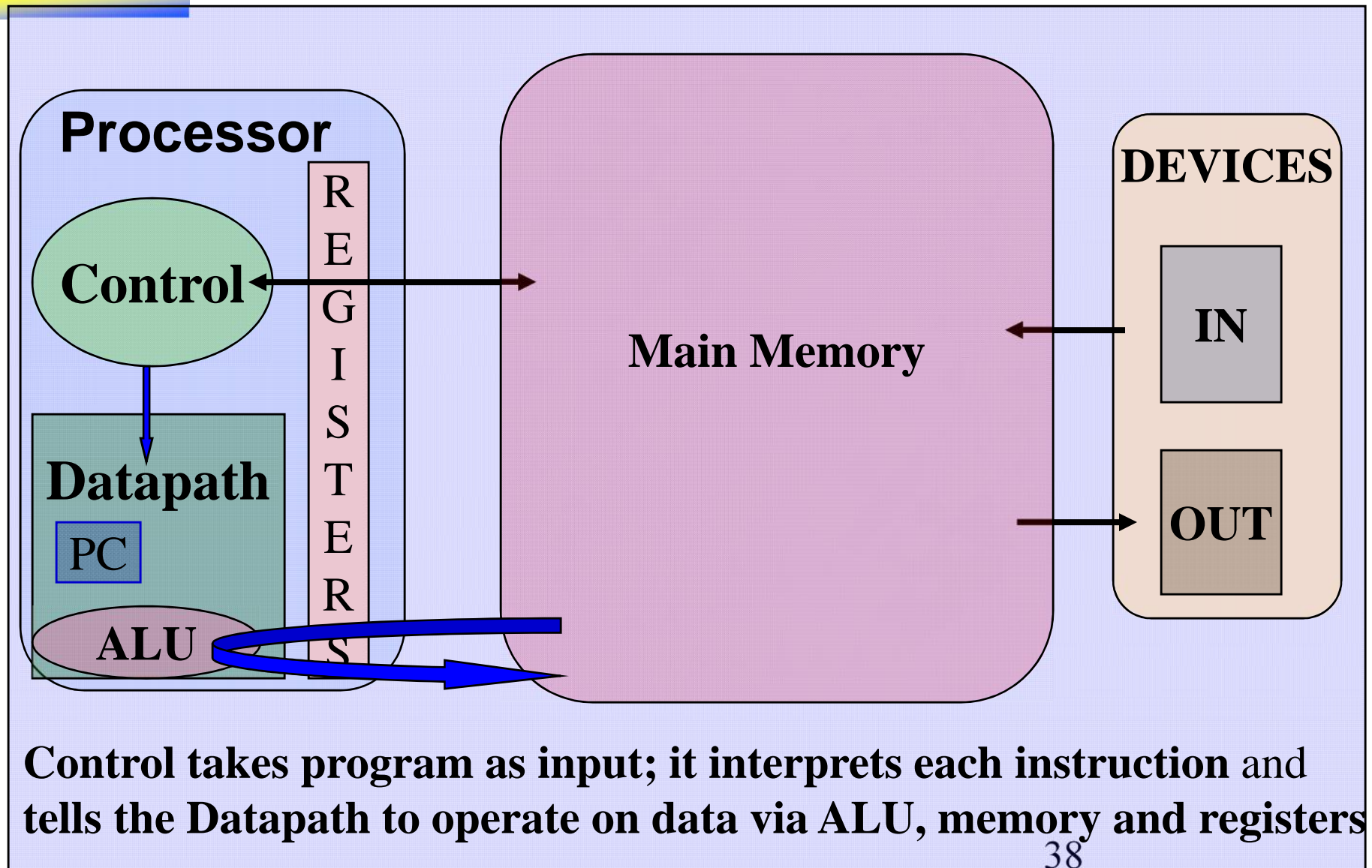CPU Control and Datapath Execute Instruction Set



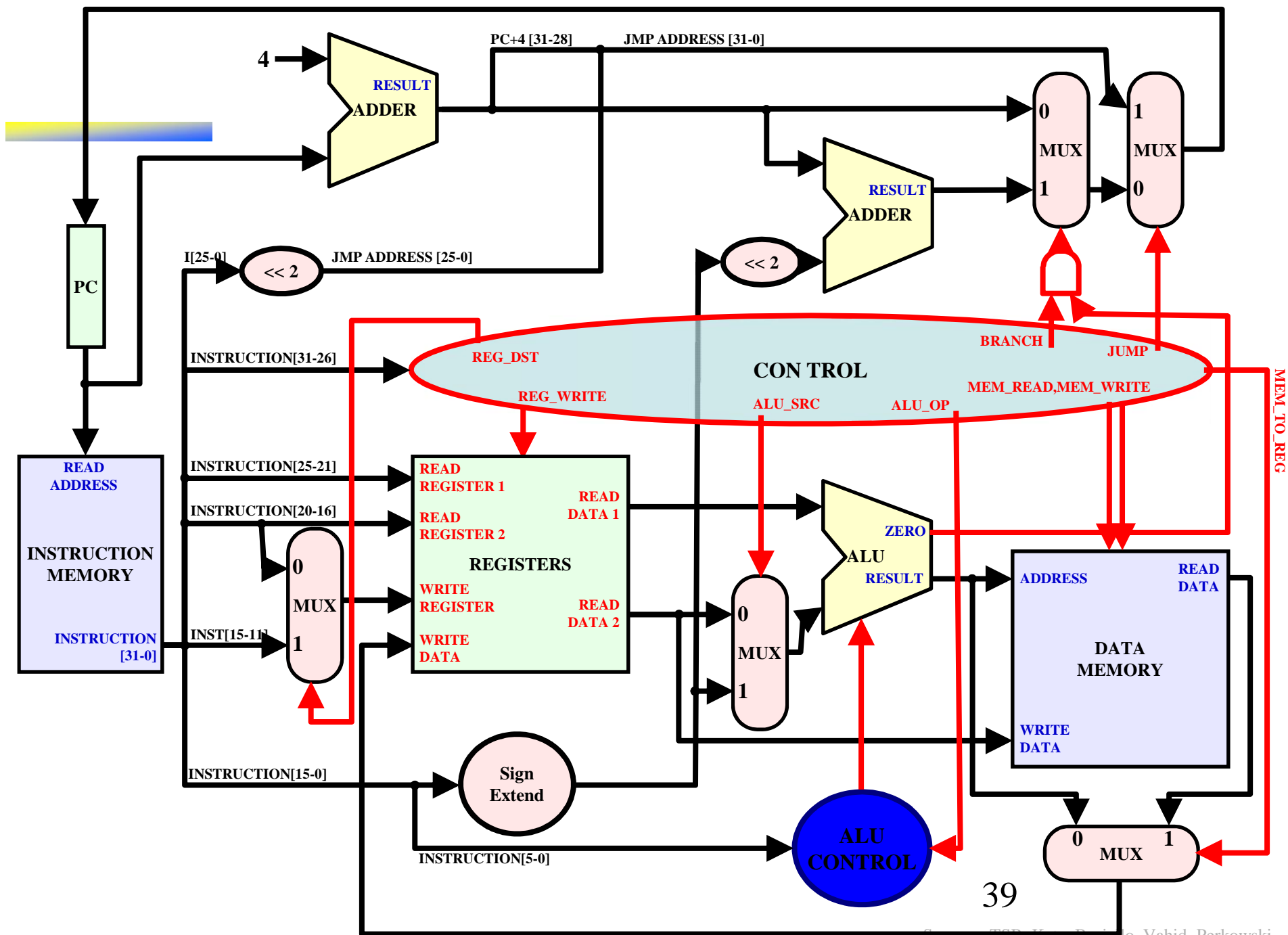

CPU Components – Single Cycle Execution

Assumptions:

- Every machine language instruction happens in 1 Clock Cycle
- MIPS architecture
 - **Microprocessor without interlocked pipeline stages**
 - reg-reg architecture: all operands must be in registers (total 24)
 - 3 Instruction Types; each instruction 32 bits long
 1. R-type: all data in registers (most arithmetic and logical)
e.g. add \$s1, \$s2, \$s3
 2. I-type: branches, memory transfers, constants
e.g. beq \$s1, \$s2, Label; lw \$s1, 32(\$s2)
 3. J-type: jumps and calls
e.g. j Label;

add \$s0, \$s1, \$s2

000000	10001	10010	10000	00000	100000
--------	-------	-------	-------	-------	--------


0	17	18	16	0	32 ⁴⁰
---	----	----	----	---	------------------

R-type Instruction: reg-reg ALU ops (e.g. add, and)

Tells operation to be performed

Tells specific variant of operation (e.g. add/sub have same opcode)

R-type Instruction

 

ADD \$S1, \$S2, \$S3


ADD RD, RS, RT

Source Register 1
(attached to “Read Register 1” input)


Source Register 2
(attached to “Read Register 2” input)


Shift amount (for sll, srl etc.)

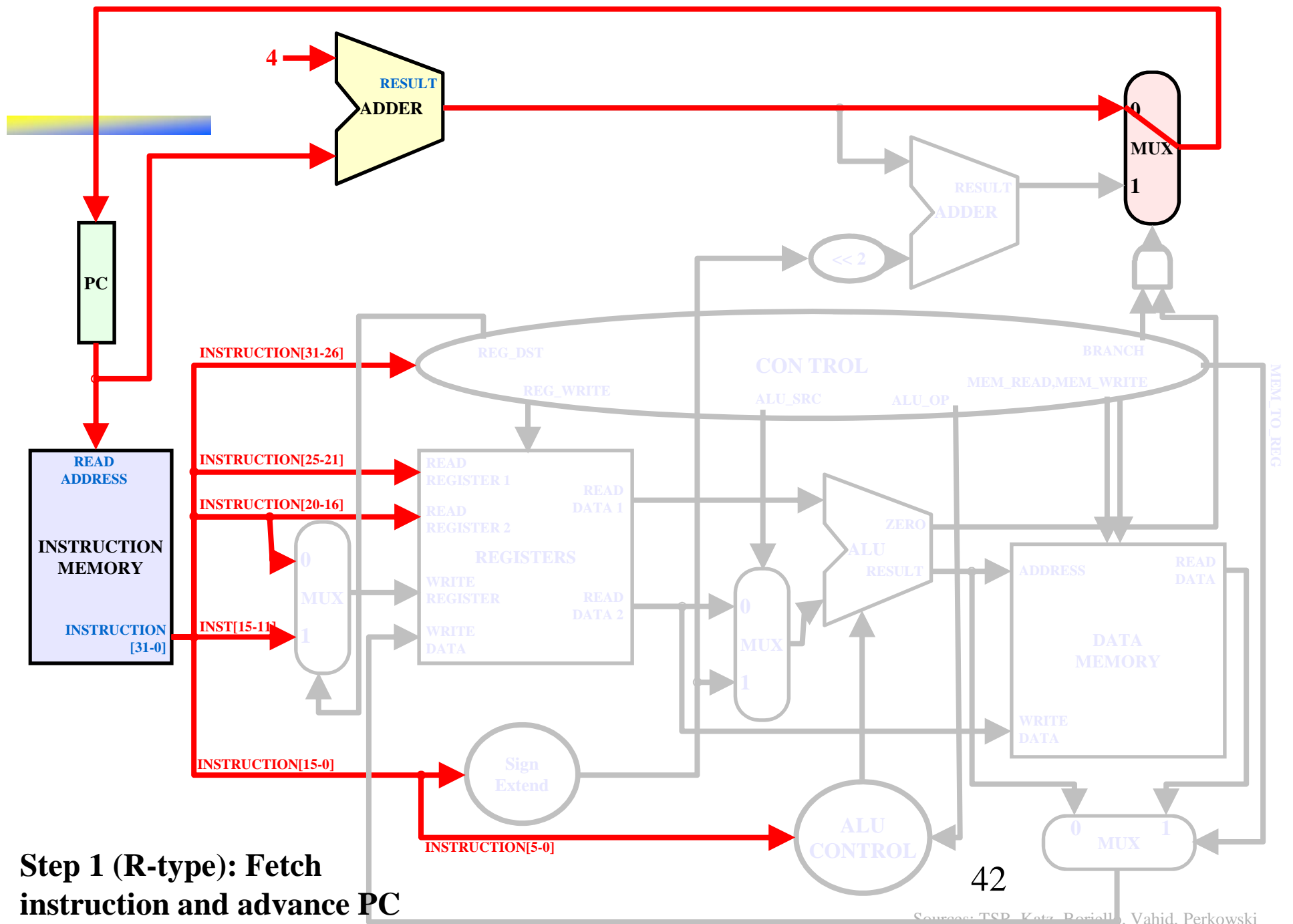
Destination Register
(attached to “Write Register” input)



42

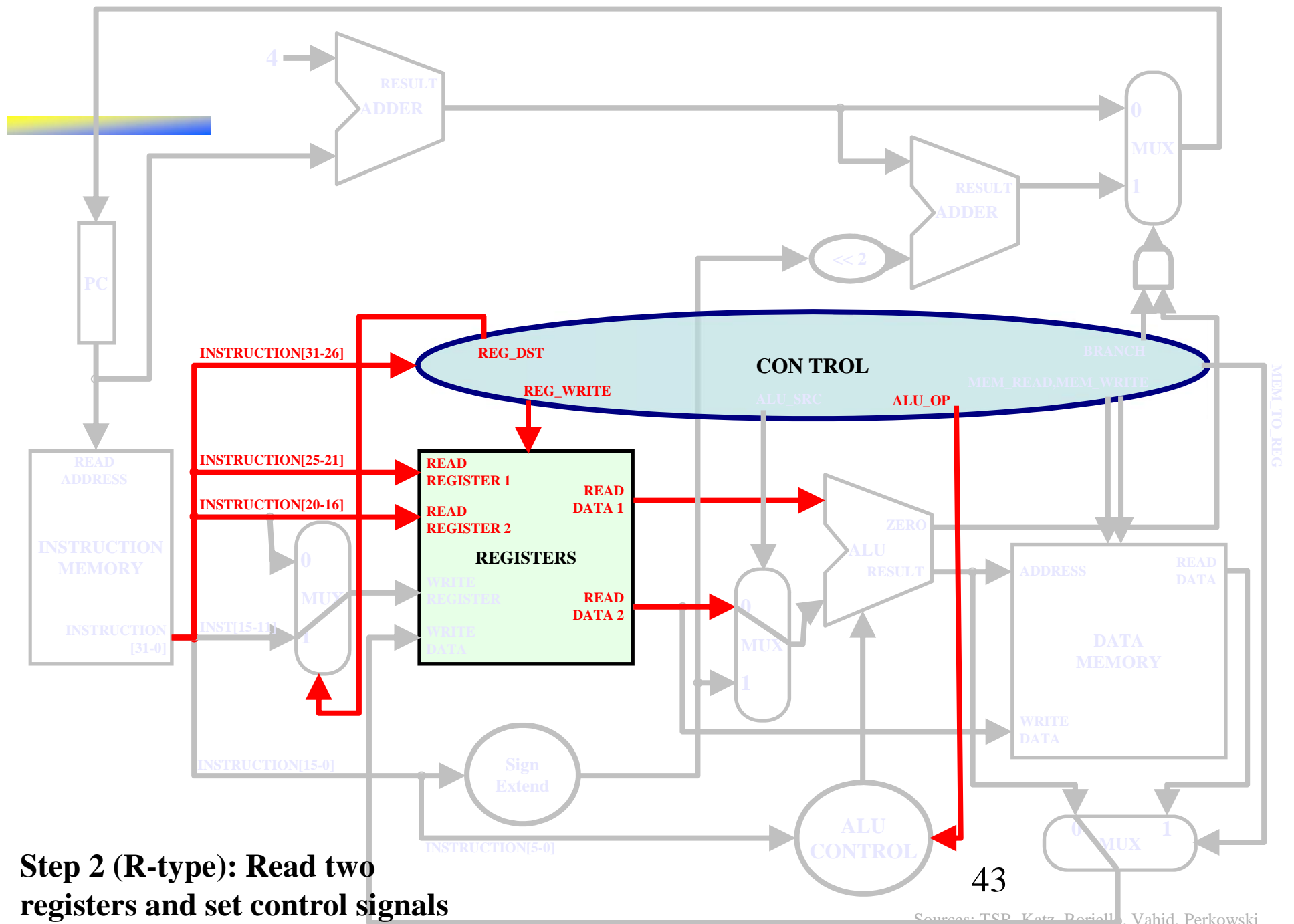


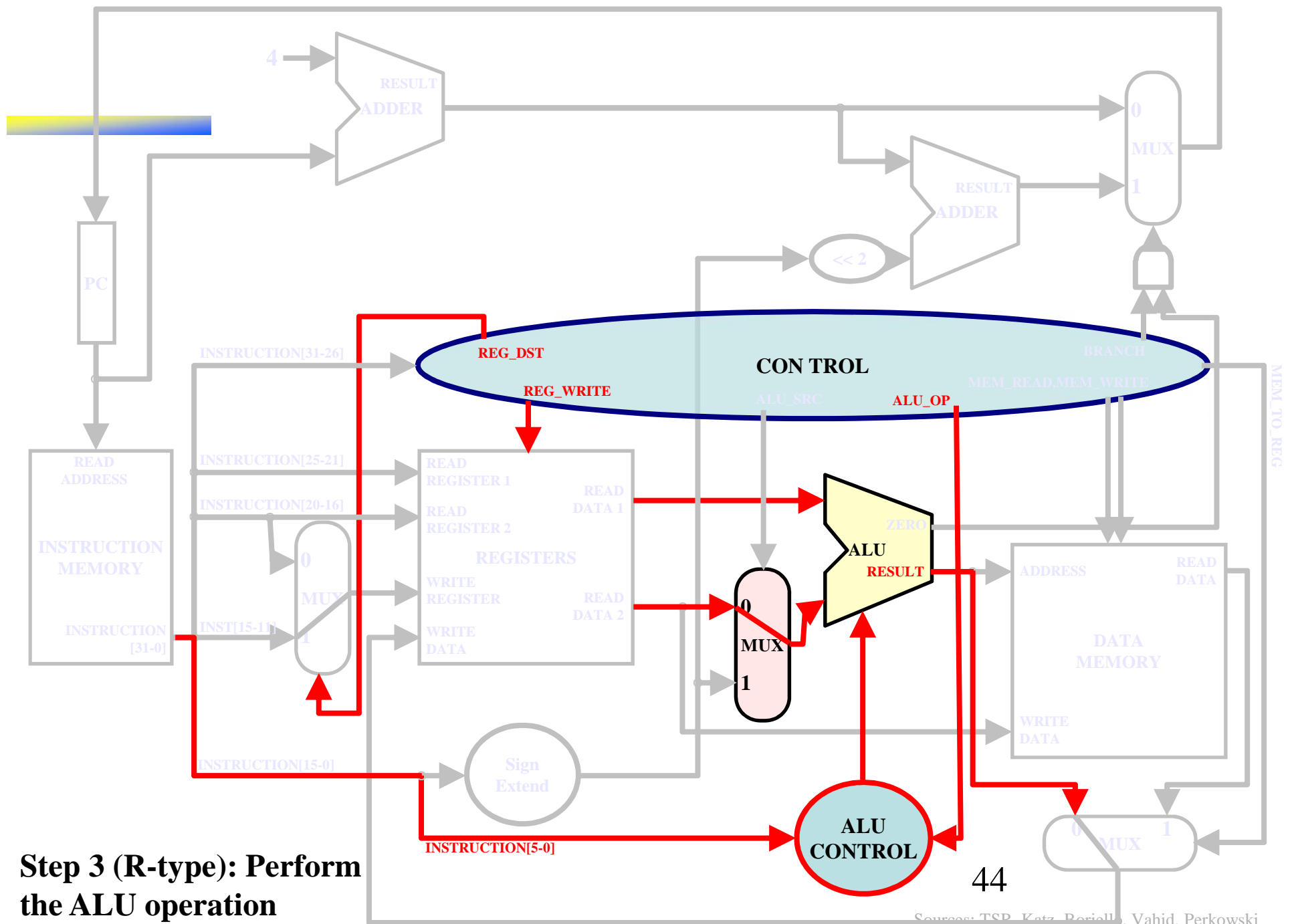

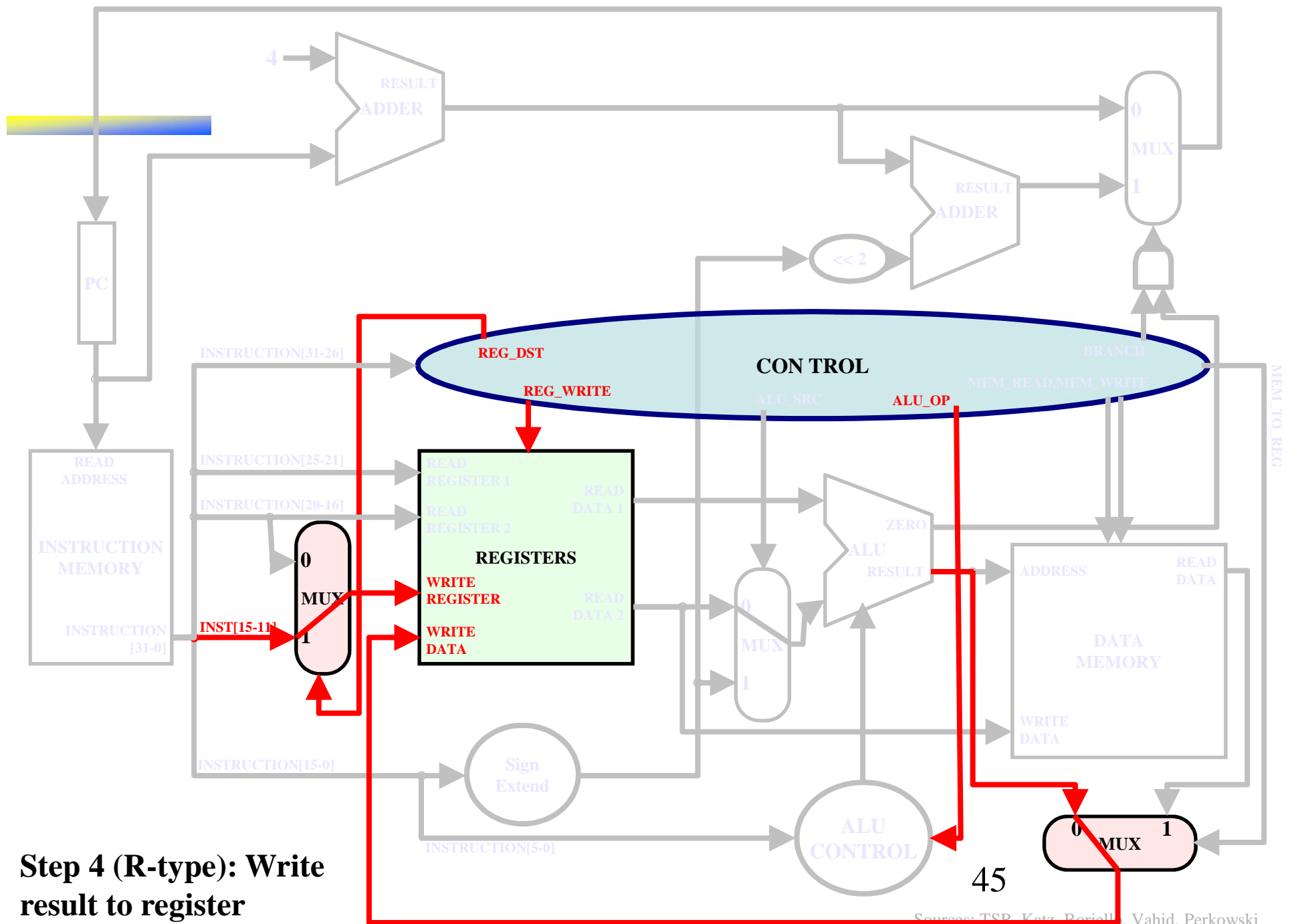

I-Type: Store Instruction

Tells operation to be performed

 

Base Address Register
(attached to “Read Register 1” input)


Source register
whose value will be
stored to memory
(attached to “Read Register 2” input)

Constant offset
(added to the base
address in RS)

SW \$S1, 32(\$S2)


SW RT, #(RS)

*Note: same as x86
MOV [ebx+32], eax*

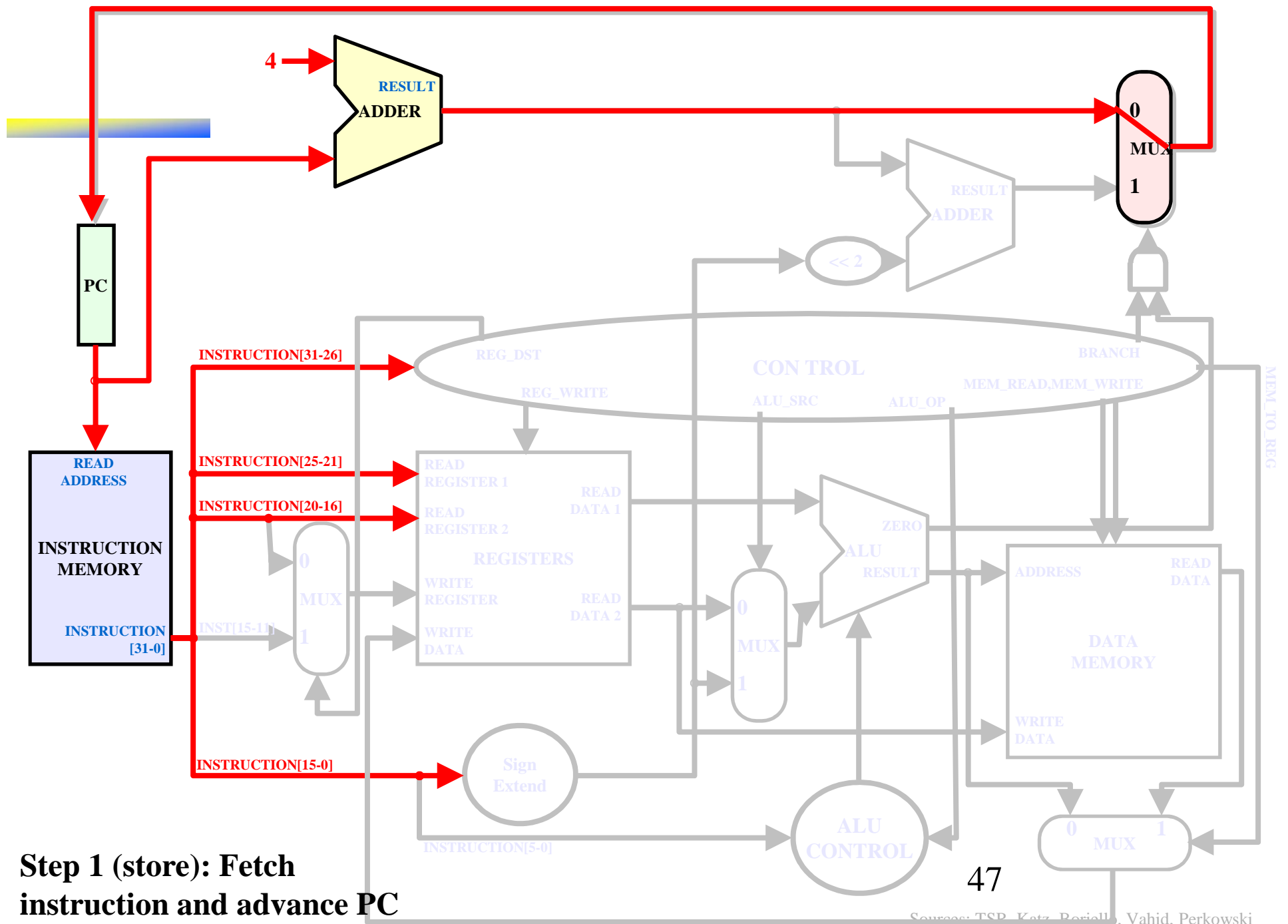




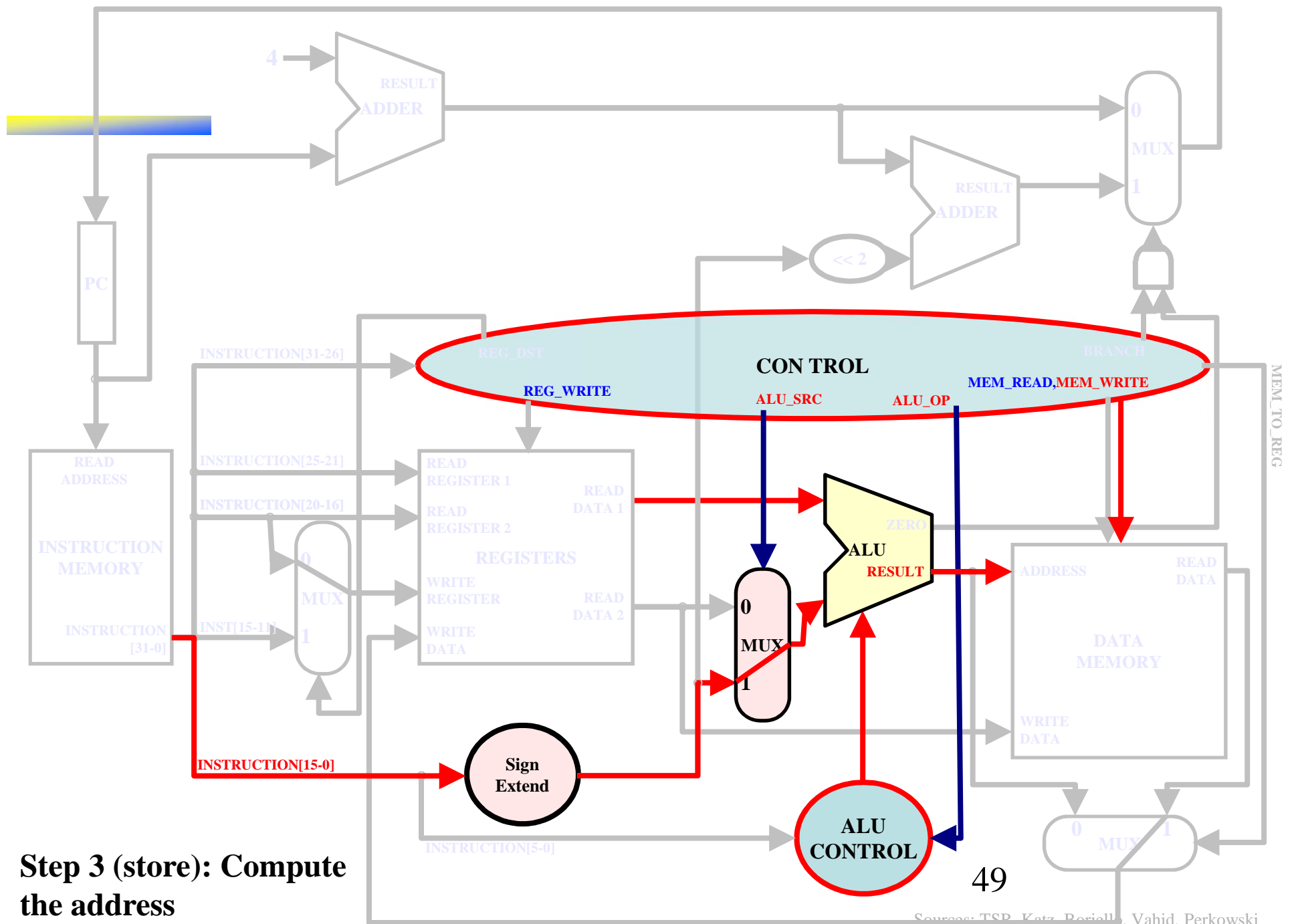Sources: TSP, Katz, Periell, Vahid, Perkowski




Step 3 (store): Compute the address

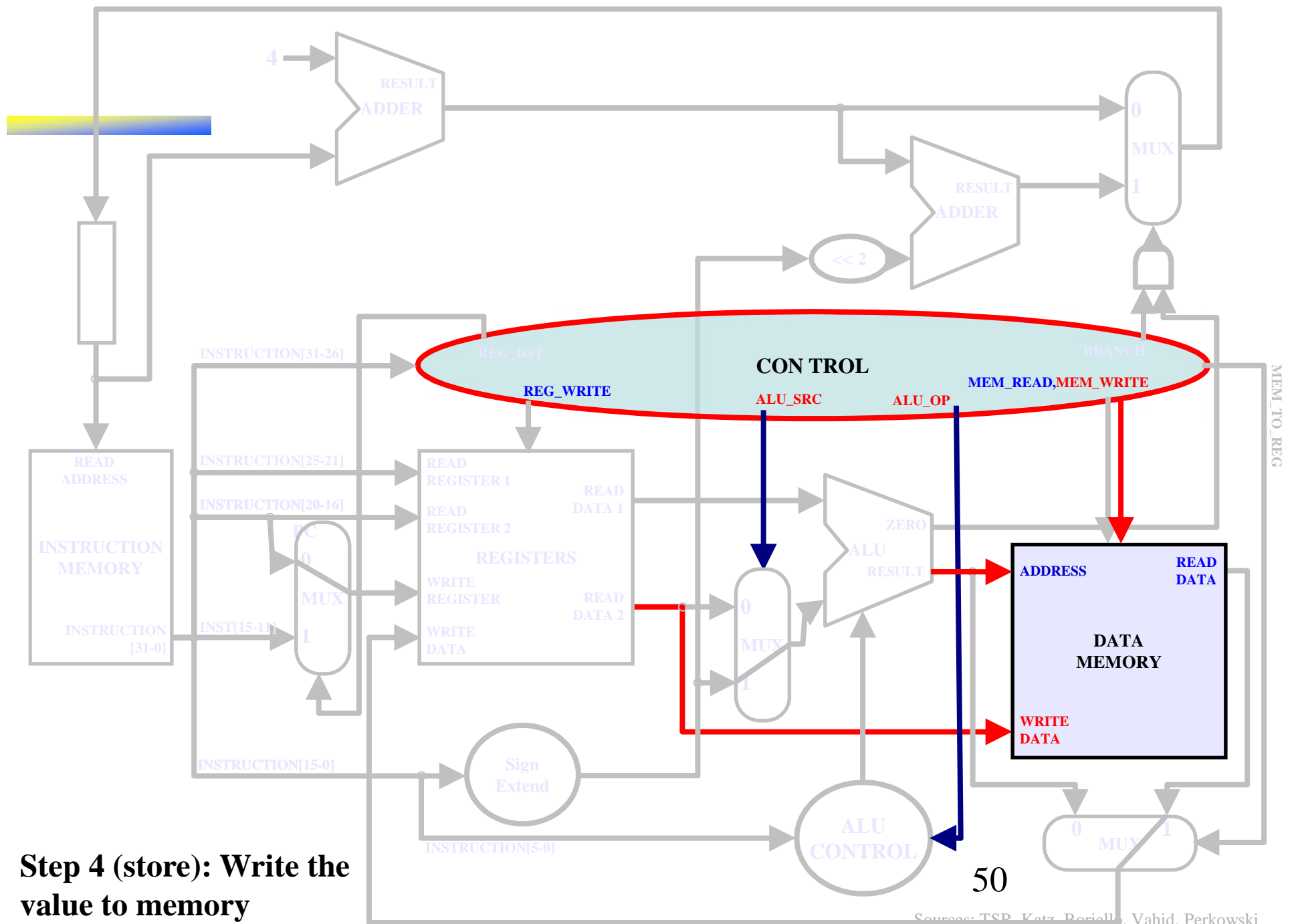

I-Type: Conditional Branch

BEQ/BNE Instruction

 

31-26

25-21

20-16

15-0

Source Register 1
(attached to “Read
Register 1” input)


Source register 2
(attached to “Read
Register 2” input)

Word Offset, which
we multiply by 4 (via
<<2) to get Bit Offset,
then add to PC+4 to
get the address of the
instruction to which
we branch if RS = RT)
“PC-relative address”

BEQ Source1, Source2, Offset


BEQ \$S1, \$S2, 100 = AL

4 17 18 25 = ML (in binary)

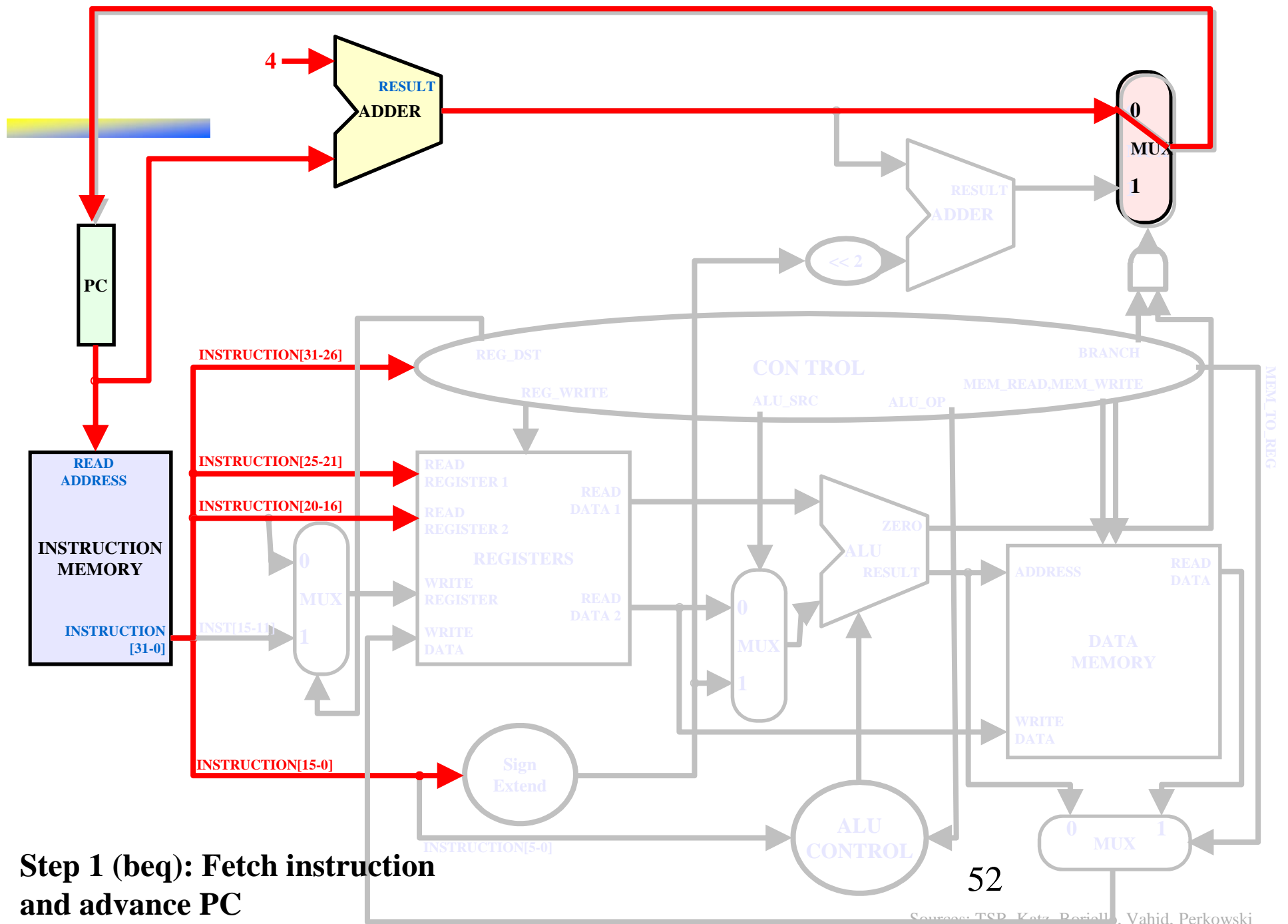

52



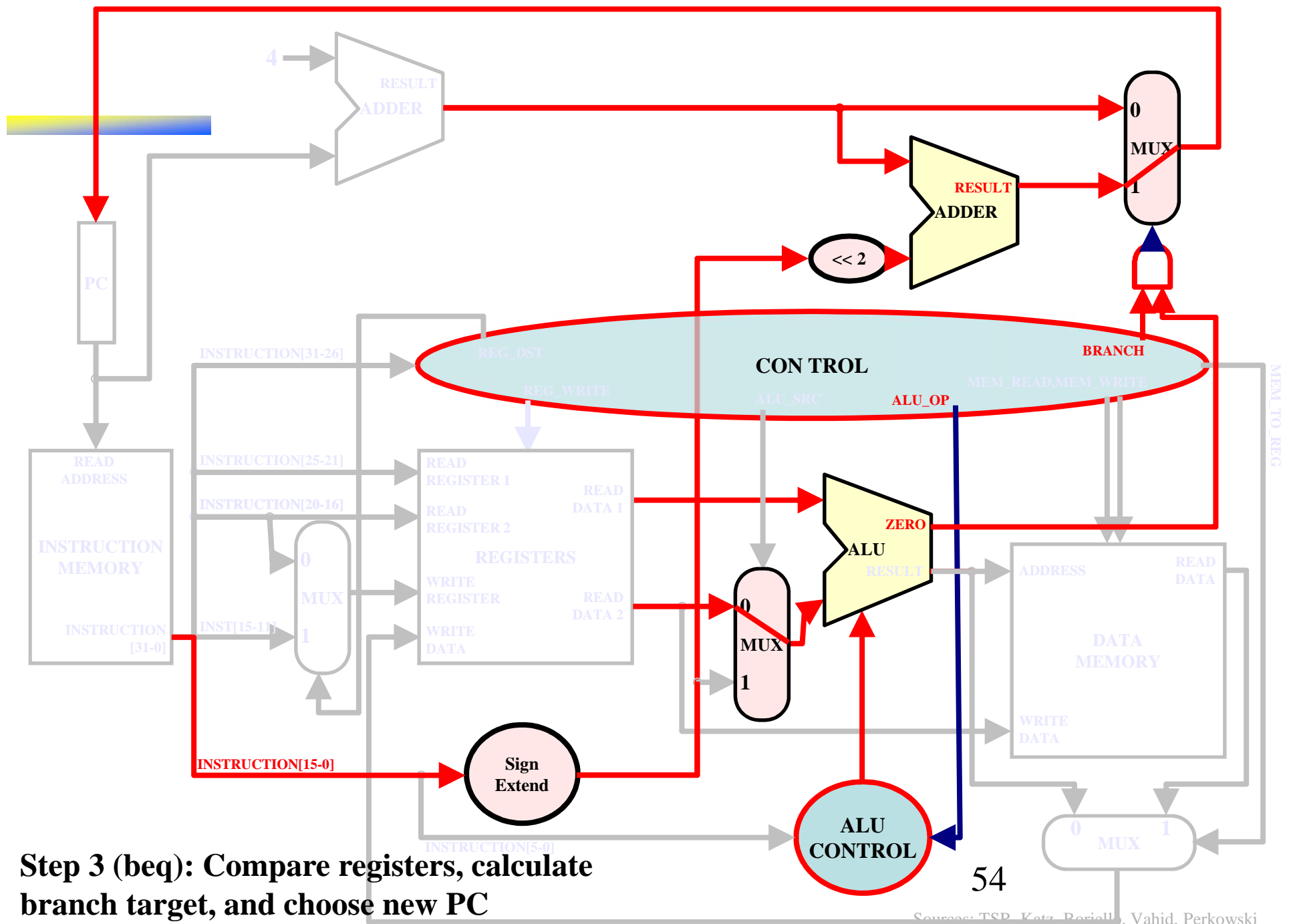

J-Type: Unconditional Branch

**JMP/JAL
Instruction**

OPCODE = 2 or 3	BRANCH TARGET ADDRESS
--------------------	-----------------------

31-26

25-0

J Offset

J 10000 = AL

2 2500 = ML (in binary)

Actual Address (in words) which we multiply by 4 ($\ll 2$) to get 28-Bit Address, then concatenate to upper 4 bits of PC+4 to get the 32-bit address of instruction to which we branch unconditionally

